



QST



ARRL Periodicals Archive - Search Results

A membership benefit of ARRL
and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for non-members. For members, TIS can send the photocopies immediately and include an invoice. Non-members must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on DVD: Annual DVDs are available for recent publication years. For details and ordering information, visit www.arrl.org/benefits.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.


For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Sep 1994

Title: Easy Dual-Band VHF/UHF Antenna, An

[Click Here to Report a Problem with this File](#)

ARRL Periodicals on DVD

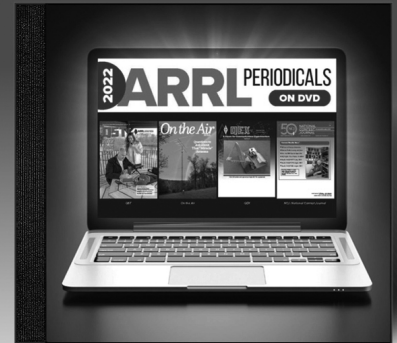

ARRL's popular journals are available on a compact, fully searchable DVD. Every word and photo published in *QST*, *On the Air*, *QEX*, and *National Contest Journal (NCJ)* during 2022 is included!

- **SEARCH** the full text of every article by entering titles, call signs, names--any word.
- **SEE** every word, photo (most in color), drawing and table in technical and general-interest features, columns, and product reviews, plus all advertisements.
- **PRINT** what you see or copy it into other applications.

In addition, the DVD includes source code for software projects and PC board patterns, Section News, Contest Soapbox and Results.

ARRL Item No. 1694

Retail Price \$24.95

Order online at arrl.org/shop



ARRL
The National Association for
Amateur Radio®

An Easy

Dual-Band VHF/UHF

Antenna

You've just opened the box that contains your new H-T and you're eager to get on the air. But the *rubber duck* antenna that came with your radio is not working well. Sometimes you can't reach the local repeater. And even when you can, your buddies tell you that your signal is noisy.

If you have 20 minutes to spare, why not build a low-cost *J-pole* antenna that's guaranteed to outperform your rubber duck? My design is a dual-band J-pole. If you own a 2-meter/70-cm H-T, this antenna will improve your signal on *both* bands.

Hams throughout the world have built and used J-pole antennas for years. My design is simple, lends itself to experimentation and alternative construction techniques, and has the following features:

- A 1.7:1 SWR or better throughout most of the 2-meter band and less than 2:1 across the 70-cm band.
- Easy set up. You can put it on the air in a matter of seconds, or store it in a space no larger than a small paperback book.
- Simple construction. The entire antenna system can be built in less than 30 minutes using TV twin lead and coaxial cable.

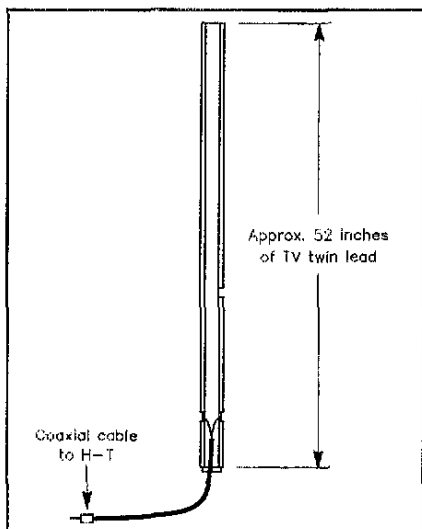


Figure 1—The J-pole antenna is approximately 52 inches long and may be hung from just about anywhere.

Why settle for the performance your rubber duck antenna offers?

Build this portable J-pole and boost your signal for next to nothing!

By Jim Reynante, KD6GLF
PO Box 27856
San Diego, CA 92198

All of the SWR data in this article was measured at the transmitter end of the feed line. The reference impedance is 50 Ω, since most equipment is designed for this impedance.

J-Pole Antenna Theory

The J-pole is a vertically polarized antenna with two elements: the radiator and the matching stub. Although the antenna's radiator and stub are 1/4 wavelength and 1/4 wavelength, respectively, it operates as an end-fed half-wave antenna. Here's how you determine the lengths of the J-pole's two elements:

$$L_{3/4} = \frac{8856 \times V}{f}$$

$$L_{1/4} = \frac{2952 \times V}{f}$$

where:

$L_{3/4}$ = the length of the 3/4-wavelength radiator in inches

$L_{1/4}$ = the length of the 1/4-wavelength stub in inches

V = the velocity factor of the TV twin lead
 f = the design frequency in MHz

These equations are more straightforward than they look. Just plug in the numbers and go. My design assumes that 146 MHz is the center frequency on the 2-meter band. You may, of course, substitute a center frequency of your choice. Even though the antenna is designed using a 2-meter center frequency, it also works well on 70 cm—as you'll see later.

Don't let the *velocity factor* throw you. The concept is easy to understand. Put simply, the time required for a signal to travel down a length of wire is *longer* than the time required for the same signal to travel the same distance in free space. This delay—the *velocity factor*—is expressed in

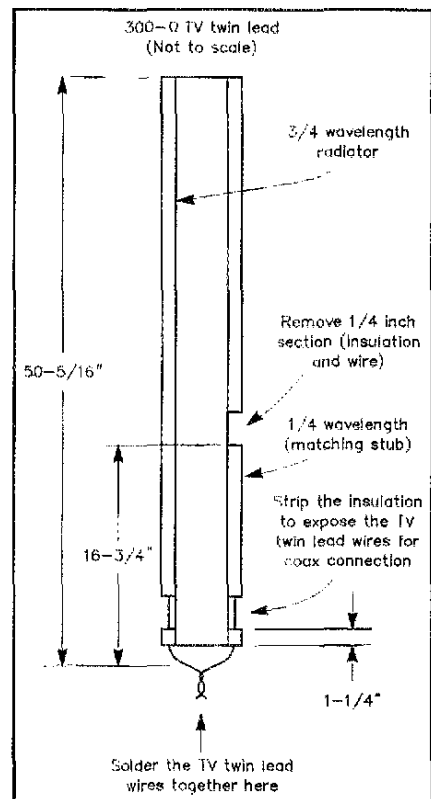


Figure 2—The basic J-pole layout. Note the areas where insulation and/or wire must be trimmed.

terms of the speed of light, either as a percentage or a decimal fraction. Knowing the velocity factor is important when you're building antennas and working with transmission lines. Because of the delay, 360° of a given signal wave exists in a physically shorter distance on a wire than in free space. This shorter distance is the *electrical* length, and that's the length we need to be concerned about.

Copper wire has a velocity factor of about 0.93, whereas TV twin lead has a velocity factor of 0.81 to 0.85 depending on who made it. If you're unsure about the twin lead you're using, just use 0.85 as its velocity factor. It's okay if it turns out to be too high. You'll be able to compensate by trimming the antenna. (It's better for the antenna to be too long than too short!) The TV twin lead I used had a velocity factor of 0.83. So, using the formulas, at 146 MHz the lengths would be approximately 50³/₁₆ inches for the 3/4-wavelength radiator and 16³/₁₆ inches for the 1/4-wavelength stub.

Construction

Because of the few materials needed to construct this antenna, you'll find it surprisingly easy to build. Start with approximately five feet of 300-Ω TV twin lead and about six feet of 50-Ω coaxial cable (see Figure 1) with a suitable connector (most H-T's use a BNC connector). Use only flat 300-Ω TV twin lead, not foam core. RF can potentially short through the foam core.

Start by stripping off 1/2 inch of insulation at one end of the TV twin lead (see Figure 2). Solder the two exposed wires together. This is the bottom of the antenna. Next, measure up 1¹/₄ inches from the soldered wires and remove the insulation from the twin lead to expose 1/8 to 1/4 inch of wire on both sides. Be careful not to nick or break these wires... They are your connection points for the coaxial feed line.

Now you're ready to measure and cut the elements of the antenna. On one side of the twin lead, measure up 50³/₁₆ inches from the center of the exposed wire and trim off the twin lead entirely (both conductors). This side of the twin lead is the radiator of the J-pole antenna. On the opposite side of the twin lead, measure up 16³/₁₆ inches from the center of the exposed wire and carefully remove a 1/4-inch section of insulation and wire. This is the 1/4-wavelength matching stub.

Turn your attention to the coaxial cable and strip the end without the connector. Separate and expose the center conductor from the braided shield. Attach the coax to the twin lead by soldering the center conductor of the coax to the longer element of the J-pole and the shield to the shorter of the two elements. Do this at the point where you removed the twin lead insulation and exposed the wire on both sides (see Figure 3).

Apply a generous amount of weatherproof silicon sealant to the exposed coax to prevent moisture from seeping into the line. Now tape the coax to the twin lead to relieve

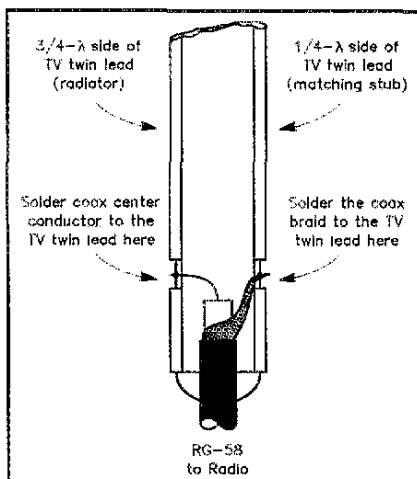


Figure 3—The coaxial feed line is connected directly at the antenna. Be careful to observe that the center conductor is soldered to the side of the TV twin lead with the longer conductor. The braid is connected to the side with the shorter conductor.

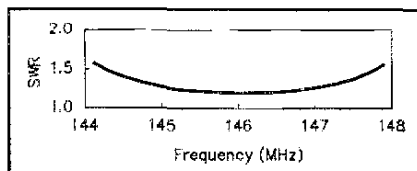


Figure 4—The SWR of the J-pole over the 2-meter band.

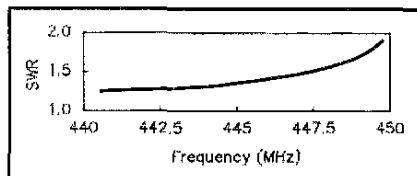


Figure 5—On the 70-cm band, the J-pole still presents a useable SWR.

strain on the soldered connection points. Heat shrink tubing also works well for this application.

Tuning

Hang your J-pole vertically by making a small hole at the top of the antenna and tying a length of twine or fishing line. Take care to keep the antenna away from metal objects that could detune it.

Tuning the J-pole is easy. Using a high-accuracy VHF/UHF SWR meter (borrow one if necessary), simply trim the length of the elements until you read a 1:1 SWR—or as close as you can get. Trim in very small increments; don't chop off an inch at a time! Remember to trim in a 3:1 ratio to maintain the 3/4- to 1/4-wavelength proportions. For example, if you cut 1/8 inch from the 1/4-wavelength stub, you must cut 3/8 inches from the 3/4-wavelength radiator ($1/8 \times 3 = 3/8$).



I should mention that this design can cause RF coupling to the feed line. To avoid this, you can place ferrite beads on the coax at the feedpoint. An alternative is to use 3 to 5 turns of coax (1 to 2 inches in diameter) to create an RF choke at the feedpoint.

Results

Figure 4 shows my SWR measurements on 2 meters. As you can see, the antenna displayed a fairly flat SWR over most of the 2-meter band. At no point did it exceed 1.7:1. I achieved slightly higher, but useable, results on 70 cm (see Figure 5).

After hanging my J-pole from a tree limb and connecting my H-T, I switched to the frequency of a nearby repeater and gave it a try. I was able to talk with several local hams and they all said my signal sounded strong and clear. So far so good, but now came the true test. I switched to a repeater located about 17 miles north of my home, one that I couldn't use with my rubber duck antenna. I keyed the transceiver, announced my call sign, and was almost immediately greeted by a friendly voice. It worked! And not only that, it worked pretty well. The other ham said I was full-quieting into the repeater. Not bad for less than 30 minutes of work. Reception performance was also improved.

Summary

A J-pole antenna will never replace a beam or a full-size vertical mounted at 30 feet, but it offers relatively good performance for a minimum of materials, time and effort.

The applications of this antenna go beyond emergency or portable use. A permanent weatherproof enclosure can be built by mounting the J-pole inside a length of PVC tubing capped at the top. The PVC tube may then be placed at the top of a mast or similar structure. You can drill a small hole in the side of the PVC tube for the coax. Just make sure to seal it against the weather. The PVC will protect the antenna and can be painted to match the color of your house or apartment. If you live in an area where you can't put up outside antennas, hang the J-pole in your attic! If the antenna is located more than 10 feet from your radio, use a low-loss coaxial feed line such as RG-213 or equivalent.

Because of the low cost, simple construction, compact size and improved performance, there's no reason not to build several of these antennas. Keep one rolled up in your backpack when hiking, or in the glove compartment of your car! □